


555 Timer IC

1

* It's an IC that can operate as either monostable or astable multivibrator.


Monostable

⇒ One-shot multivibrator.

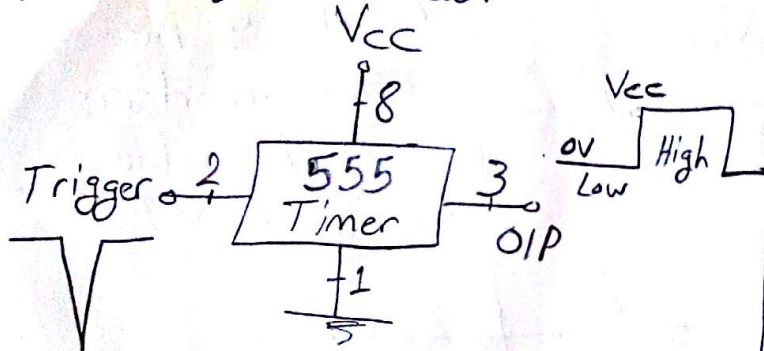


Astable

⇒ Free-running multivibrator.

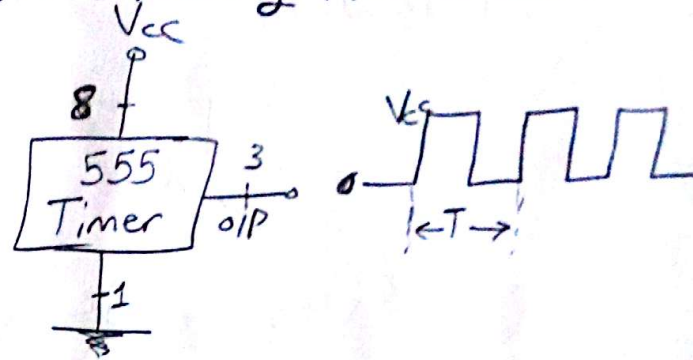

* Block Diagram:-

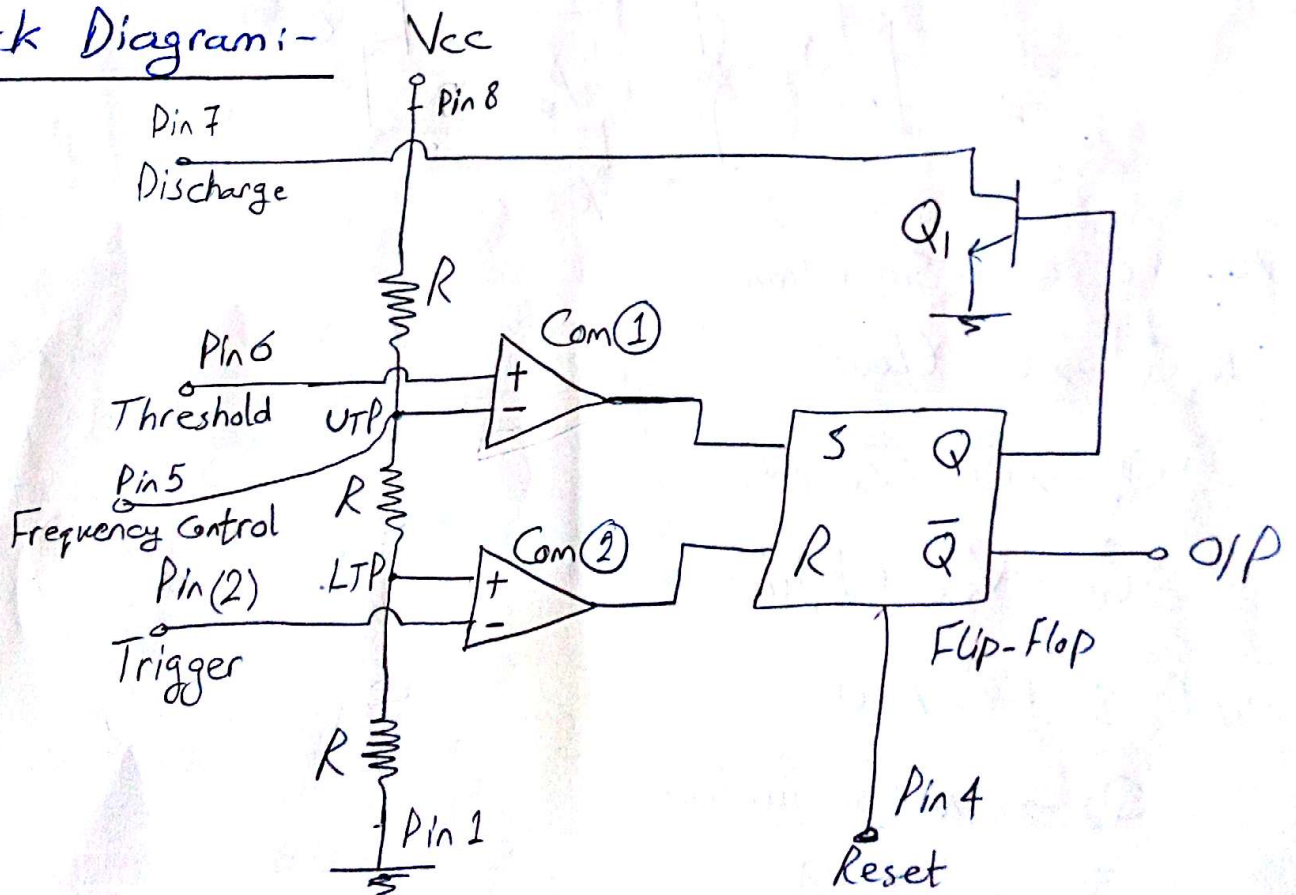


$$V_{UTP} = \frac{2V_{CC}}{3} \rightarrow \text{Upper Trigger Point}$$


$$V_{LTP} = \frac{V_{CC}}{3} \rightarrow \text{Lower Trigger Point}$$

* RS Flip-Flop :-

S	R	Q	\bar{Q}
0	0	No change	
0	1	0	1
1	0	1	0
1	1	Not Allowed	

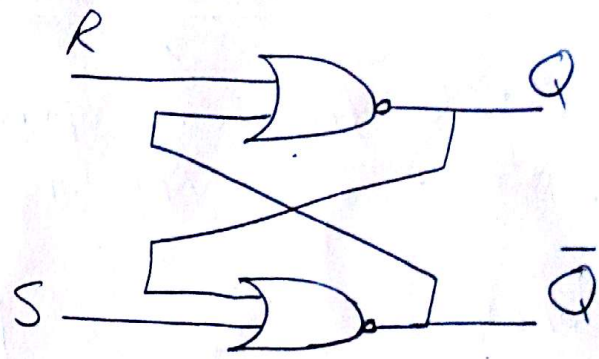

↳ May be considered as a bistable MVT.

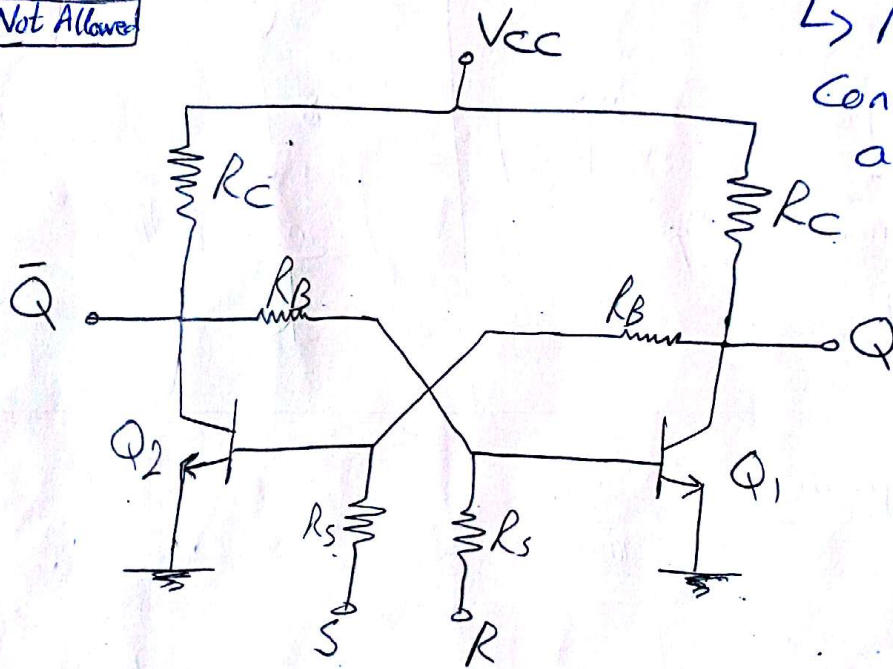

① Assume $Q_1 \rightarrow$ Saturation

$\therefore Q \rightarrow 0$ (Low)

$\therefore Q_2 \rightarrow$ off (cutoff)

$\therefore \bar{Q} = V_{cc}$ (High)

\Rightarrow If $S=1$, $R=0$

$\therefore Q_2 \rightarrow$ ON (saturation)

$\therefore \bar{Q} \approx 0$ (Low)

$\therefore Q_1 \rightarrow$ off


$Q \approx V_{cc}$ (High)

$$\therefore Q \approx 0 \text{ (Low)}$$

$\therefore Q_2 \Rightarrow$ ~~on~~ off (cutoff)

$$\therefore \bar{Q} \approx V_{CC} \text{ (High)}$$

* Monostable 555 :-

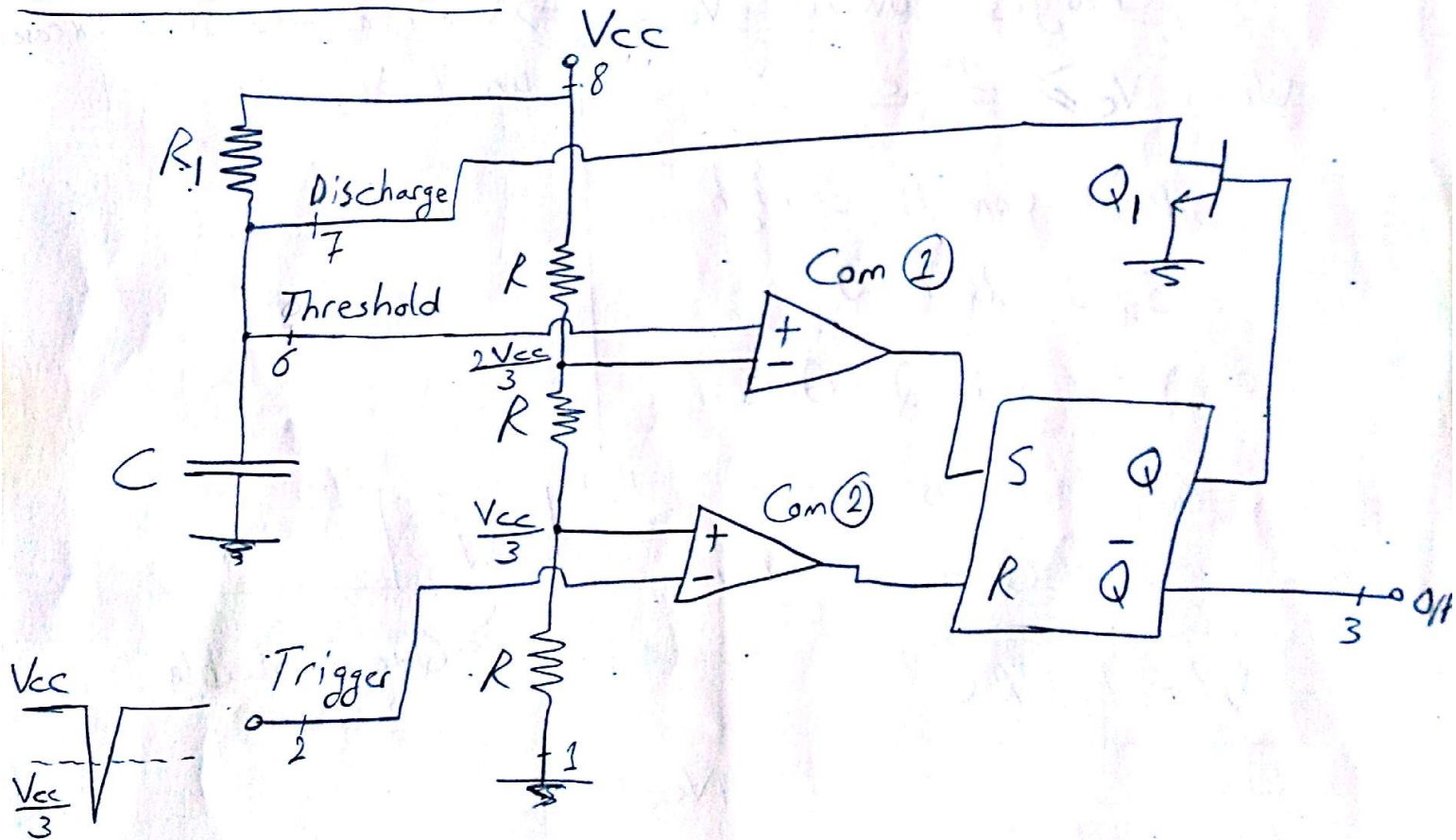

\Rightarrow Assume $Q = \text{Logic } 1$ & $\bar{Q} = \text{Logic } 0$:

$\therefore Q_1 \rightarrow \text{Saturation}$

$$\therefore V_C = 0$$

⇒ When Trigger is Applied:

If $V_{Trigg} > \frac{V_{CC}}{3} \Rightarrow$ Comparator ② O/P is Low

O/P of Com ① is low

If $V_{Trigg.} < \frac{V_{CC}}{3}$

4*

∴ O/P of Comparator ② is High

∴ R = Logic high

∴ R = 1 & S = 0

∴ Q = 0, $\bar{Q} = 1$

∴ Q₁ → Cutoff

∴ C charges towards V_{CC}

When $V_C \geq \frac{2V_{CC}}{3}$

∴ O/P of Com ① is high

∴ S = 1 & R = 0

∴ Q = 1 & $\bar{Q} = 0$

∴ Q₁ → Saturation


∴ C ~~charges~~ discharges through the BJT path.

∴ O/P of com ① becomes Low

⇒ V_C continues to decrease until V_C = 0.


⇒ The output is as follows:

→ \bar{Q}

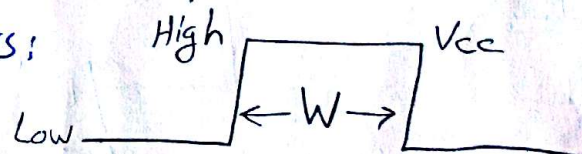


→ Quasi-Stable State.

$$W = 1.1 RC$$

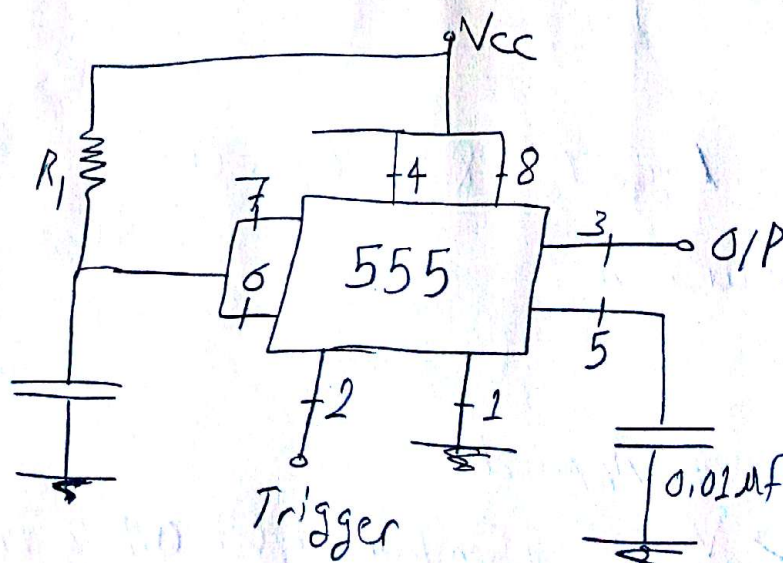

* Astable 555 Operation:-

5

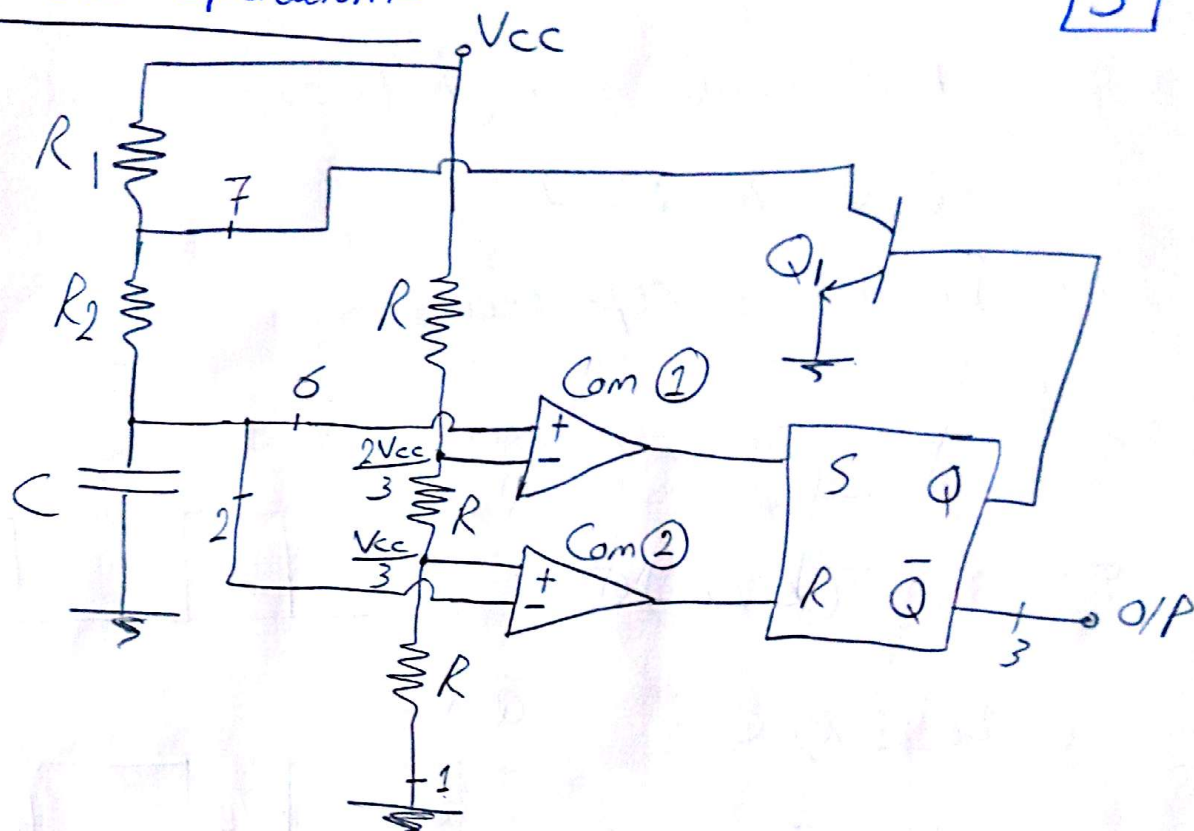

⇒ Assume $Q = 0$ & $\bar{Q} = 1$

∴ $Q_1 \rightarrow \text{Off}$

∴ C charges through (R_1 & R_2) towards V_{cc}

$V_C > \frac{V_{cc}}{3} \Rightarrow \text{O/P of Com(2) is Low (R=0)}$

When $V_C > \frac{2V_{cc}}{3}$

∴ O/P of Com(1) is high ($S=1$)

∴ $S=1$ & $R=0$

∴ $Q=1$ & $\bar{Q}=0$

∴ $Q_1 \Rightarrow \text{ON}$

∴ C discharges through R_2

∴ O/P of Com(1) is Low ($S=0$) → No change

⇒ When $V_C < \frac{V_{CC}}{3}$

∴ O/P of $G_m(2)$ is high ($R=1$)

∴ $Q=0$ & $\bar{Q}=1$

The process is repeated.

⇒ The O/P & V_C waveforms:


$$T_H = 0.693(R_1 + R_2)C$$

$$T_L = 0.693 R_2 C$$

$$\Rightarrow T = T_H + T_L$$

$$= 0.693(R_1 + 2R_2)C$$

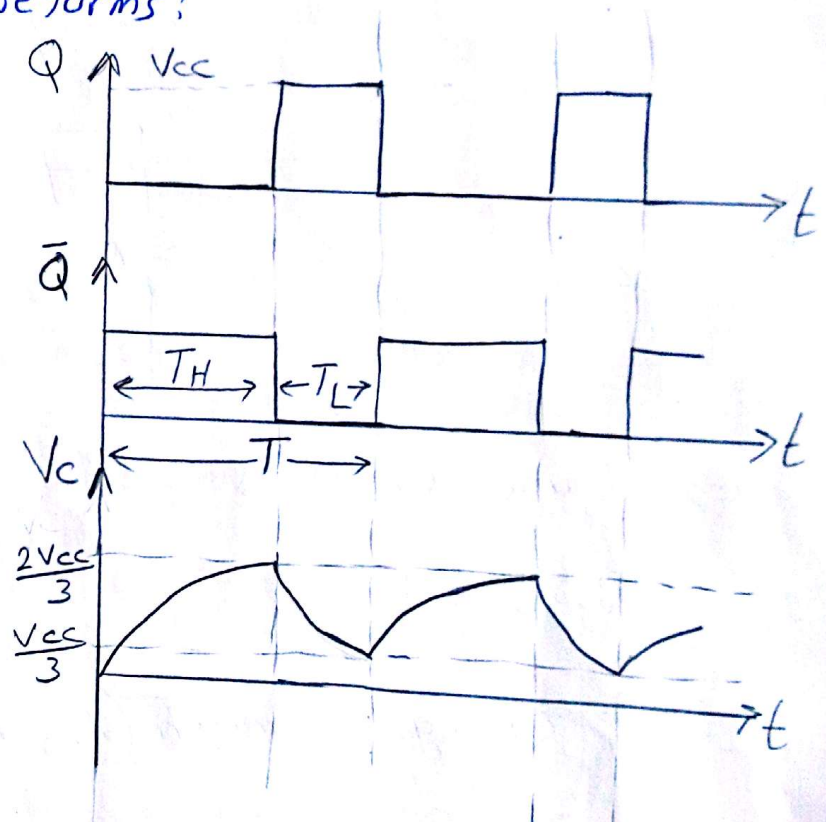
$$\Rightarrow f = \frac{1}{T} = \frac{1.44}{(R_1 + 2R_2)C}$$



$$\Rightarrow \text{Duty Cycle: } D = \frac{T_H}{T_H + T_L} = \frac{R_1 + R_2}{R_1 + 2R_2}$$

⇒ For 50% duty cycle: Choose R_1 ~~very~~ to be very small
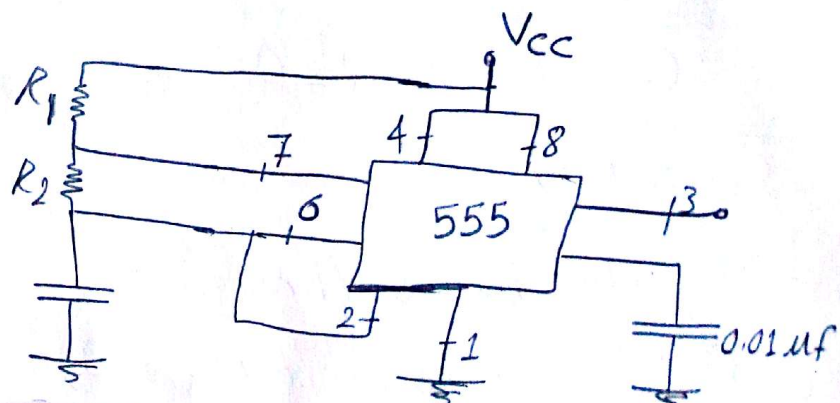
$$D \approx \frac{R_2}{2R_2} = \frac{1}{2}$$




(1) For the monostable 555 circuit previously explained;
if $C = 0.5 \text{ nF}$

Find the value of R so that the output pulse has a width of $10 \text{ } \mu\text{s}$.

Solution

$$W = 1.1 RC$$

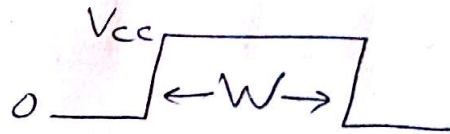

$$\therefore 10 \times 10^{-6} = 1.1 \times 0.5 \times 10^{-9} \times R$$

$$\therefore R = 18.18 \text{ k}\Omega$$

(2) For the Astable circuit:

$$C = 680 \text{ pF}$$

O/P is square wave with $f = 20 \text{ kHz}$

$$D = 80\%$$

Find R_1 & R_2

Solution

$$D = \frac{R_1 + R_2}{R_1 + 2R_2}$$

$$\therefore 0.8 = \frac{R_1 + R_2}{R_1 + 2R_2}$$

$$\therefore 5(R_1 + R_2) = 4(R_1 + 2R_2) \Rightarrow R_1 = 3R_2 \rightarrow \textcircled{1}$$

$$F = 20 \text{ kHz}$$

8

$$\therefore T = \frac{1}{20 \times 10^3} = 50 \mu\text{s}$$

$$\therefore T = 0.093 C(R_1 + 2R_2)$$

50 μs

$$\therefore 50 \times 10^{-6} = 0.093 \times 680 \times 10^{-12} (3R_2 + 2R_2)$$

$$\therefore R_2 = 21.31 \text{ k}\Omega$$

$$\therefore R_1 = 63.93 \text{ k}\Omega$$